

# Discussion 07

## Single Cycle Datapath

Aditya Balasubramanian

`aditbala [at] berkeley [dot] edu`

# Announcements

# Agenda

- SDS Review
- Single Cycle Datapath



# Definitions (Pt. 1)

- Clk
  - Central timing unit of the entire SDS; usually only one clock per system
- State element
  - Any clocked element: stores values
  - Only does computation things at the rising edge of the clock
  - E.g. registers
- Logic element
  - Any unclocked elements: does not store value
  - Computes ALL THE TIME!
  - E.g. combinatorial logic elements (AND gates, OR gates, etc.)

## Definitions (Pt. 2)

- Flip-flop
  - state element that stores 1 bit's value (0/1)
- Register
  - **n**-bit state element; created with **n** chained FFs
  - **D** = input; **Q** = output
  - Reads value from **D** at clock tick, puts value into **Q**


# Definitions (Pt. 3)

- Rising clock edge (RCE)
  - clk goes from 0  $\Rightarrow$  1; Usually instantaneous
  - Triggers all the state elements dependent directly on the clock
- Falling clock edge  
clk goes from 1  $\Rightarrow$  0
- Setup time
  - Time BEFORE RCE where input must be stable
- Hold time
  - Time AFTER RCE where input must be stable
- Clock-to-q time (c2q)
  - Time after RCE needed for value in Q to change
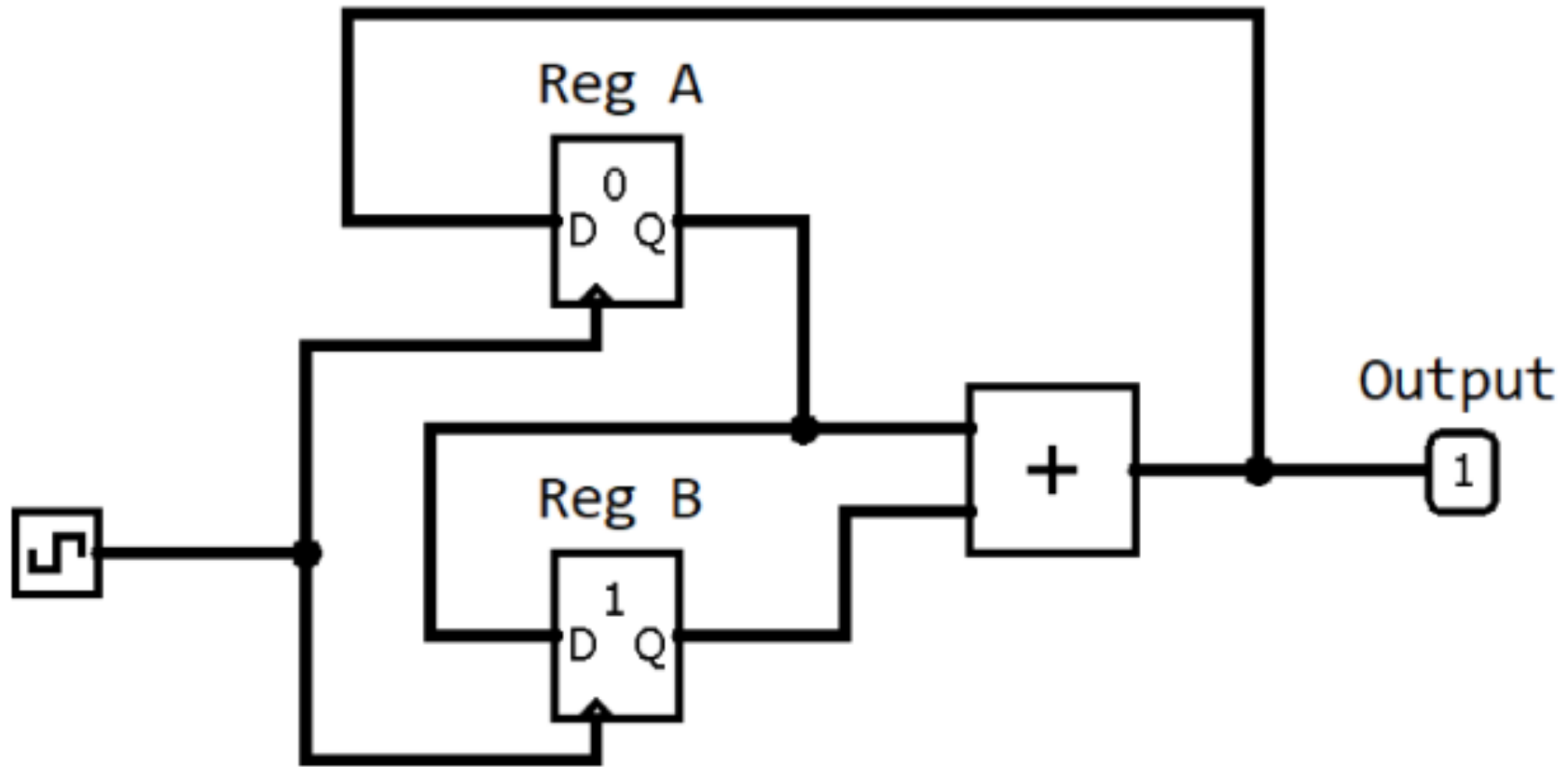
# Definitions (Pt. 4)

- Combinational logic delay
  - Combinatorial delay between 2 state elements
  - Usually Sum of total delays within the path from the Q of one register to the D of another (or the same) register
- Critical path
  - Total delay between 2 state elements
  - Clk-to-q (reg1) + longest CL + setup time (reg2)
- Maximum clock frequency
  - $1 / \text{minimum clock period}$





# Equations

$$\text{max hold time} \leq t_{\text{clock to q}} + \text{shortest CL}$$

- Any longer of a hold time means that value has potential to change

$$\text{cycle time} \geq t_{\text{clock to q}} + \text{longest CL} + t_{\text{setup}}$$

- Cycle time = clock period
- Any shorter cycle time means the values may not finish computing correctly in time

# Single Cycle Datapath

# What Even is a datapath?

- Given a program counter (the address of the instruction we need to execute)
- Update the registers to reflect the given instruction
- Every single update we need to make will be in the RISC-V Reference Card: VERY USEFUL
- Standard datapath accounts for all real RISC-V 32bit instructions
- No pseudoinstructions

# Datapath Basics

- Wiring accounts for flow of data
- Control logic block does the hard work of "thinking"
- CL takes data/signal in from datapath  $\Rightarrow$  arrows point towards control logic
  - Instr[31:0]; BrEq; BrLT
- CL feeds signal back to datapath  $\Rightarrow$  arrows point away from control logic
  - Calculates signals to tell datapath what components of datapath to use
  - All other signals in standard datapath

# Stages of a Single Cycle Datapath

# Instruction Fetch (IF)

## 1. Update the value in PC

- (**PCSel** = 0)  $PC = PC + 4$
- (**PCSel** = 1)  $PC = \text{ALU output}$

## 2. Fetch instruction from IMEM at PC

- IMEM is “Instruction memory”, generally in the code section!

# Instruction Decode (ID)

1. Parse instruction from 32 bits binary into useful signals
2. Access RegFile with `rs1`, `rs2`, and `rd`
  - a. We can obtain the register numbers from the reference card  
RegFile output the data that is read
  - b. Access ImmGen using **ImmSel**
3. Generates immediate based on instruction type, and pad them to made full 32 bits



# Execute (EX)

- ALU Operation using ALUSel
  - Inputs to the ALU:
    - (ASel = 0): Use `R[rs1]`
    - (ASel = 1): Use `PC`
    - (BSel = 0): Use `R[rs2]`
    - (BSel = 1): Use `Immediate`
  - Does regular ALU operations (for `I` and `R` type instructions)
  - Also does all the adding! (except for `PC + 4`)
- OR Branch Comparator
  - (**BrUn** = 0) Compare `R[rs1]` and `R[rs2]` signed
  - (**BrUn** = 1) Compare `R[rs1]` and `R[rs2]` unsigned
  - Outputs **BrEq** and **BrLt**

# Memory Access (Mem)

## 1. Access DMEM (Data Memory)

### a. Inputs:

- i. Addr: address we're accessing, calculated by ALU
- ii. DataW: data we want to put into memory; only used for **s** type instructions
- iii. (**MemRW** = 0) do not write into memory
- iv. (**MemRW** = 1) write into memory

# Write Back (WB)

- Selects which value to write to `rd`
  - Inputs:
    - (**WBSEL** = 0) Data Memory that is read (with appropriate editing depending on whether we have `lb`, `lh`, `lw`)
    - (**WBSEL** = 1) ALU Output
    - (**WBSEL** = 2) PC + 4
- Output a value that goes into DataD of RegFile
  - **RegWEn** determines whether we actually update `rd`

# Control Signals

Control Signal	Signal	Used for	Example
PCSel (Will never be *)	0	PC = PC + 4 Normal Instruction Flow; default next PC	No edit to PC in description
	1	PC = ALU Output J type instructions; B type instructions if branch is taken	jalr <b>PC = rs1 + imm</b>
ImmSel	I, I*, S, B, U, J	Identify how to generate the immediate (bits to use, how to extend, how to piece the bits together)	
	*	The immediate is not used	add <b>rd = rs1 + rs2</b>
RegWEn (Will never be *)	0	No writeback to RegFile allowed (we don't need to update rd)	beq <b>if (rs1 == rs2) PC = PC + offset</b>
	1	Update rd	add <b>rd = rs1 + rs2</b>
BrUn	0	Signed Branch Comparisons	bge
	1	Unsigned Branch Comparisons	bgeu
	*	Branching is not used	Any none B-type instruction

# Control Signals Pt. 2

Control Signal	Signal	Used for	Example	
ASel	0	Operate on rs1	add	<b>rd = rs1 + rs2</b>
	1	Operate on PC	beq	<b>PC = PC + offset</b>
	*	A is not used in ALU; Only B is used in ALU Output; lui and auipc	lui	<b>rd = imm</b>
BSel	0	Operate on rs2	add	<b>rd = rs1 + rs2</b>
	1	Operate on imm	addi	<b>rd = rs1 + imm</b>
ALUSel	Various	Identify which ALU Operation		

# Control Signals Pt. 3

Control Signal	Signal	Used for	Example
MemRW (Will never be *)	0	No writing to memory	Everything except for stores
	1	Write to memory	Sb, sh, sw
WBSel	0	rd = memory output; used for load instructions	lb, lh, lw
	1	rd = ALU output	add <b>rd = rs1 + rs2</b>
	2	rd = PC + 4 for jal and jalr exclusively	jal <b>rd = PC + 4</b>
	*	We don't write back to rd Exclusively when RegWEn == 0	

# Thank you!