

# Discussion 06

**Boolean Logic, SDS, FSM**

Aditya Balasubramanian

`aditbala [at] berkeley [dot] edu`

# Announcements

# Agenda

- Boolean Logic
- SDS
- FSM

# Boolean Logic

# Boolean Logic

- Truth table: describes all possible behaviors of a circuit
  - Left values = input;
  - Right values = output
- $AB = A \& B$  (A and B)
- $A + B = A \parallel B$  (A or B)
- $\sim A$  (not A)

# SDS

# Definitions (Pt. 1)

- Clk
  - Central timing unit of the entire SDS; usually only one clock per system
- State element
  - Any clocked element: stores values
  - Only does computation things at the rising edge of the clock
  - E.g. registers
- Logic element
  - Any unclocked elements: does not store value
  - Computes ALL THE TIME!
  - E.g. combinatorial logic elements (AND gates, OR gates, etc.)

## Definitions (Pt. 2)

- Flip-flop
  - state element that stores 1 bit's value (0/1)
- Register
  - **n**-bit state element; created with **n** chained FFs
  - **D** = input; **Q** = output
  - Reads value from **D** at clock tick, puts value into **Q**




# Definitions (Pt. 3)

- Rising clock edge (RCE)
  - clk goes from 0  $\Rightarrow$  1; Usually instantaneous
  - Triggers all the state elements dependent directly on the clock
- Falling clock edge  
clk goes from 1  $\Rightarrow$  0
- Setup time
  - Time BEFORE RCE where input must be stable
- Hold time
  - Time AFTER RCE where input must be stable
- Clock-to-q time (c2q)
  - Time after RCE needed for value in Q to change
 
# Definitions (Pt. 4)

- Combinational logic delay
  - Combinatorial delay between 2 state elements
  - Usually Sum of total delays within the path from the Q of one register to the D of another (or the same) register
- Critical path
  - Total delay between 2 state elements
  - Clk-to-q (reg1) + longest CL + setup time (reg2)
- Maximum clock frequency
  - $1 / \text{minimum clock period}$



# Equations

$$\text{max hold time} \leq t_{\text{clock to q}} + \text{shortest CL}$$

- Any longer of a hold time means that value has potential to change

$$\text{cycle time} \geq t_{\text{clock to q}} + \text{longest CL} + t_{\text{setup}}$$

- Cycle time = clock period
- Any shorter cycle time means the values may not finish computing correctly in time



# FSM (Finite State Machine)

- An FSM takes in a sequence of characters (bits), and outputs another sequence of characters (bits).
- We represent a FSM by a number of states, plus transitions between the states
  - State labels don't usually have meanings
  - Arrow going from state A to B labeled input/output
    - When we're currently in state A and see input, we move on to state B and print output

# Thank you!